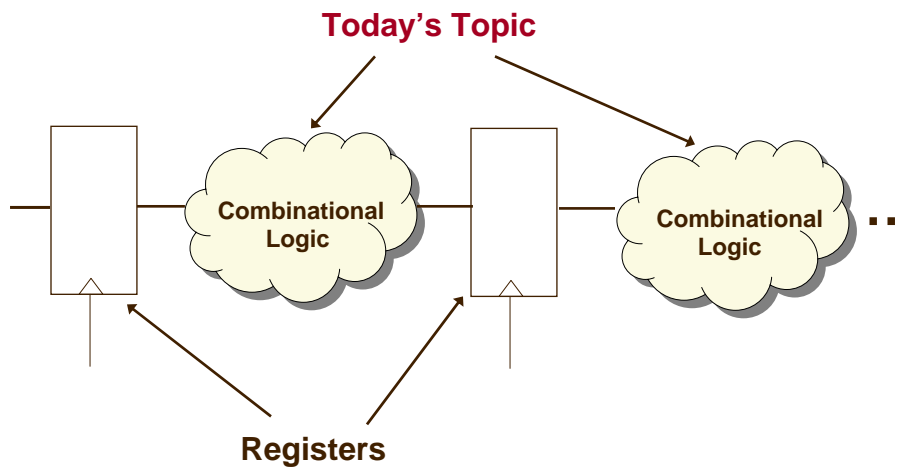



# Μοντελοποίηση Dataflow Συνδυαστικής Λογικής σε VHDL

Εισαγωγή

## Register Transfer Level (RTL) Design Description



# VHDL Design Styles

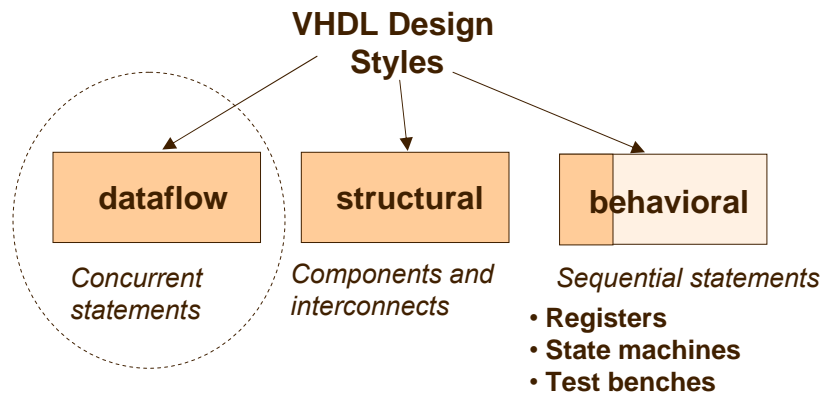

# Behavior vs Structure



An entity can be described by its *behavior* or by its *structure*, or in a mixed fashion.

*example:* a 2-input XOR gate

- Vhdl model ?

## Vhdl code

```
entity XOR is
  port ( A,B : in bit; Y : out bit);
end XOR;

architecture BEHAVIOR of XOR is
begin
  Y <= (A and not B) or (not A and B);
end BEHAVIOR;

architecture MIXED of XOR is
  component NAND
    port ( A, B : in bit; Y : out bit);
  end component;
  signal C, D, E : bit;
begin
  D <= A nand C;
  E <= C nand B;
  G1 : NAND port map (A, B, C);
  G4 : NAND port map (D, E, Y);
end MIXED;

architecture STRUCTURE of XOR is
  component NAND
    port ( A, B : in bit; Y : out bit);
  end component;
  signal C, D, E : bit;
begin
  G1 : NAND port map (A, B, C);
  G2 : NAND port map
    (A => A, B => C, Y => D);
  G3 : NAND port map
    (C, B => B, Y => E);
  G4 : NAND port map (D, E, Y);
end STRUCTURE;
```

## Signals vs Variables

```
architecture DUMMY_1 of JUNK is
  signal Y : bit := '0';
begin
  process
    variable X : bit := '0';
  begin
    wait for 10 ns;
    X := '1';
    Y <= X;
    wait for 10 ns;
    -- What is Y at this point ? Answer: '1'
    ...
  end process;
end DUMMY_1;
```

- Variables: δήλωση μέσα σε ένα Process

## Signals vs Variables

---

```
architecture DUMMY_2 of JUNK is
  signal X, Y : bit := '0';
begin
  process
  begin
    wait for 10 ns;
    X <= '1';
    Y <= X;
    wait for 10 ns;
    -- What is Y at this point ? Answer: '0'
    ...
  end process;
end DUMMY_2;
```

Signal assignments with 0 delay take effect only after a *delta* delay. *i.e.*, in the next simulation cycle.

---

## Testbenches

## Generating selected values of one input

---

```
SIGNAL test_vector : STD_LOGIC_VECTOR(2 downto 0);

BEGIN
    .....
    testing: PROCESS
    BEGIN
        test_vector <= "000";
        WAIT FOR 10 ns;
        test_vector <= "001";
        WAIT FOR 10 ns;
        test_vector <= "010";
        WAIT FOR 10 ns;
        test_vector <= "011";
        WAIT FOR 10 ns;
        test_vector <= "100";
        WAIT FOR 10 ns;
    END PROCESS;
    .....
END behavioral;
```

## Generating all values of one input

---

```
SIGNAL test_vector : STD_LOGIC_VECTOR(3 downto 0):="0000";

BEGIN
    .....

    testing: PROCESS
    BEGIN
        WAIT FOR 10 ns;
        test_vector <= test_vector + 1;
    end process TESTING;

    .....
END behavioral;
```

## Generating all possible values of two inputs

```
SIGNAL test_ab : STD_LOGIC_VECTOR(1 downto 0);
SIGNAL test_sel : STD_LOGIC_VECTOR(1 downto 0);

BEGIN
    .....

    double_loop: PROCESS
    BEGIN
        test_ab <="00";
        test_sel <="00";
        for I in 0 to 3 loop
            for J in 0 to 3 loop
                wait for 10 ns;
                test_ab <= test_ab + 1;
            end loop;
            test_sel <= test_sel + 1;
        end loop;
    END PROCESS;

    .....
END behavioral;
```

## Generating periodical signals, such as clocks

```
CONSTANT clk1_period : TIME := 20 ns;
CONSTANT clk2_period : TIME := 200 ns;
SIGNAL clk1 : STD_LOGIC;
SIGNAL clk2 : STD_LOGIC := '0';

BEGIN
    .....
    clk1_generator: PROCESS
        clk1 <= '0';
        WAIT FOR clk1_period/2;
        clk1 <= '1';
        WAIT FOR clk1_period/2;
    END PROCESS;

    clk2 <= not clk2 after clk2_period/2;

    .....
END behavioral;
```

## Generating one-time signals, such as resets

```
CONSTANT reset1_width : TIME := 100 ns;
CONSTANT reset2_width : TIME := 150 ns;
SIGNAL reset1 : STD_LOGIC;
SIGNAL reset2 : STD_LOGIC := '1';

BEGIN
.....
reset1_generator: PROCESS
    reset1 <= '1';
    WAIT FOR reset_width;
    reset1 <= '0';
    WAIT;
END PROCESS;

reset2_generator: PROCESS
    WAIT FOR reset_width;
    reset2 <= '0';
    WAIT;
END PROCESS;
.....
END behavioral;
```

## Typical error

```
SIGNAL test_vector : STD_LOGIC_VECTOR(2 downto 0);
SIGNAL reset : STD_LOGIC;

BEGIN
.....
generator1: PROCESS
    reset <= '1';
    WAIT FOR 100 ns
    reset <= '0';
    test_vector <= "000";
    WAIT;
END PROCESS;

generator2: PROCESS
    WAIT FOR 200 ns
    test_vector <= "001";
    WAIT FOR 600 ns
    test_vector <= "011";
END PROCESS;
.....
END behavioral;
```

## Wait for vs. Wait

**Wait for:** waveform will keep repeating itself forever



**Wait :** waveform will keep its state after the last wait instruction.



## Report - Examples

```
report "Initialization complete";
```

```
report "Current time = " & time'image(now);
```

```
report "Incorrect branch" severity error;
```

## Generating reports in the message window

---

```
reports: process(clk_trigger) begin
    if (clk_trigger = '0' and clk_trigger'EVENT) then
        case segments is
            when seg_0 => report time'image(now) & ": 0 is displayed" ;
            when seg_1 => report time'image(now) & ": 1 is displayed" ;
            when seg_2 => report time'image(now) & ": 2 is displayed" ;
            when seg_3 => report time'image(now) & ": 3 is displayed" ;
            when seg_4 => report time'image(now) & ": 4 is displayed" ;
            when seg_5 => report time'image(now) & ": 5 is displayed" ;
            when seg_6 => report time'image(now) & ": 6 is displayed" ;
            when seg_7 => report time'image(now) & ": 7 is displayed" ;
            when seg_8 => report time'image(now) & ": 8 is displayed" ;
            when seg_9 => report time'image(now) & ": 9 is displayed" ;
        end case;
    end if;
end process;
```

## Anatomy of a Process

---

```
[label:] process [(sensitivity list)]
    [declaration part]
begin
    statement part
end process;
```

## Sequential Statements (1)

---

- If statement

```
if boolean expression then
  statements
elsif boolean expression then
  statements
  ⋮
else boolean expression then
  statements
end if;
```

- `else` and `elsif` are optional

## Sequential Statements (3)

---

- Loop Statement

```
for i in range loop
  statements
end loop;
```

- Repeats a section of VHDL code


## Sequential Statements (2)

- Case statement
- Choices have to cover all possible values of the condition
  - Use **others** to specify all remaining cases

```
case condition is
  when choice_1 =>
    statements
  when choice_2 =>
    statements
    ⋮
  when others =>
    statements
end case;
```
 
## Παράδειγμα: Σχεδίαση ενός μετρητή

- Σχεδιάστε – υλοποιήστε σε synthesizable VHDL έναν 32-bit μετρητή με είσοδο ενεργοποίησης και ασύγχρονο reset.
- Το block διάγραμμα φαίνεται παρακάτω:



## Λύση

- Δήλωση entity:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY counter IS
  PORT (
    reset      : IN    std_logic;
    clock      : IN    std_logic;
    enable     : IN    std_logic;
    value      : OUT   std_logic_vector(31 DOWNTO 0)
  );
END counter;
```

## Λύση

- Αρχιτεκτονική του μετρητή:

```
ARCHITECTURE synthesis1 OF counter IS

  SIGNAL count : unsigned(31 DOWNTO 0); -- The unsigned type is used
                                         -- so that unsigned arithmetic
                                         -- will be synthesized


BEGIN
  PROCESS (reset, clock)
  BEGIN
    IF (reset = '1') THEN
      count <= X"00000000";
    ELSIF (clock'EVENT) AND (clock = '1') THEN
      IF (enable = '1') THEN
        count <= count + 1;
      END IF;
    END IF;
  END PROCESS;

  value <= std_logic_vector(count); -- Here, the count value is
                                    -- converted to std_logic_vector
                                    -- using a conversion function

END synthesis1;
```
 
## Παράδειγμα 2: Καταχωρητής

- Σχεδιάστε έναν 8-bit καταχωρητή σε synthesizable VHDL με είσοδο ενεργοποίησης και ασύγχρονο reset.



## Λύση 2


```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY dregister IS
    PORT( rst, clk, ena : IN      std_logic;
          d              : IN      std_logic_vector(7 DOWNTO 0);
          q              : OUT      std_logic_vector(7 DOWNTO 0) );
END dregister;

ARCHITECTURE synthesis1 OF dregister IS
BEGIN
    PROCESS (rst, clk)
    BEGIN
        IF (rst = '1') THEN
            q <= X"00";
        ELSIF (clk'EVENT) AND (clk = '1') THEN
            IF (ena = '1') THEN
                q <= d;
            END IF;
        END IF;
    END PROCESS;
END synthesis1;
```
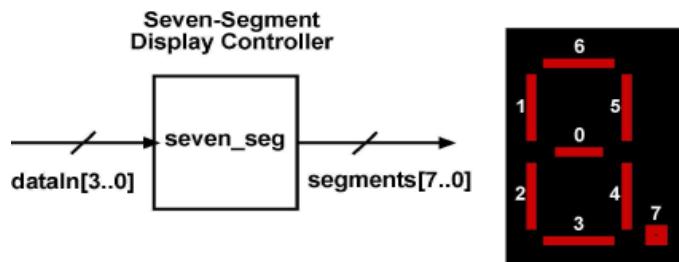
## Παράδειγμα 3 : Συνδυαστική Λογική

- Σχεδιάστε έναν ελεγκτή 7-segment-display σε synthesizable VHDL



Εισαγωγή στη VHDL

27

## Λύση

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY seven_seg IS
    PORT( dataIn      : IN      std_logic_vector(3 DOWNTO 0);
          segments    : OUT     std_logic_vector(7 DOWNTO 0) );
END seven_seg;

ARCHITECTURE synthesis1 OF seven_seg IS
    BEGIN
        WITH dataIn SELECT
            segments <=
                "10000001" WHEN "0000", -- 0
                "11001111" WHEN "0001", -- 1
                "10010010" WHEN "0010", -- 2
                "10000110" WHEN "0011", -- 3
                "11001100" WHEN "0100", -- 4
                "10100100" WHEN "0101", -- 5
                "10100000" WHEN "0110", -- 6
                "10001111" WHEN "0111", -- 7
                "10000000" WHEN "1000", -- 8
                "10000100" WHEN "1001", -- 9
                "11111111" WHEN OTHERS;

    END synthesis1;
```

Εισαγωγή στη VHDL

28