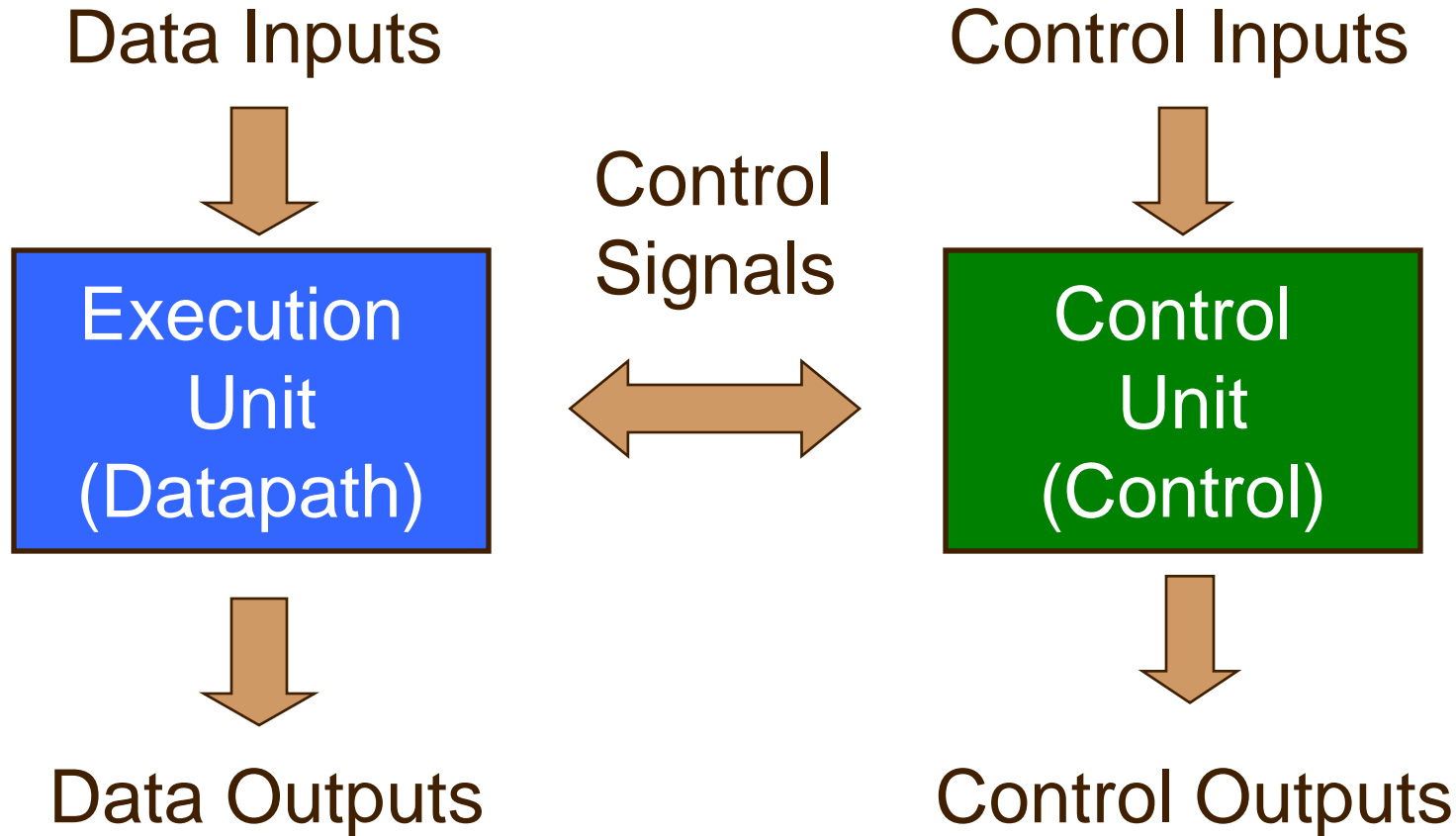


Μηχανές Πεπερασμένων Καταστάσεων σε VHDL

Δομή ενός Τυπικού Ψηφιακού Συστήματος




Finite State Machines (FSMs)

- Οποιοδήποτε κύκλωμα με μνήμη μπορεί να αναπαρασταθεί ως Finite State Machine
- Η Σχεδίαση FSMs περιλαμβάνει
 - Ορισμός καταστάσεων
 - Ορισμός μεταβάσεων μεταξύ καταστάσεων
 - Βελτιστοποίηση / ελαχιστοποίηση
- Above Approach Is Practical for Small FSMs Only


Moore FSM

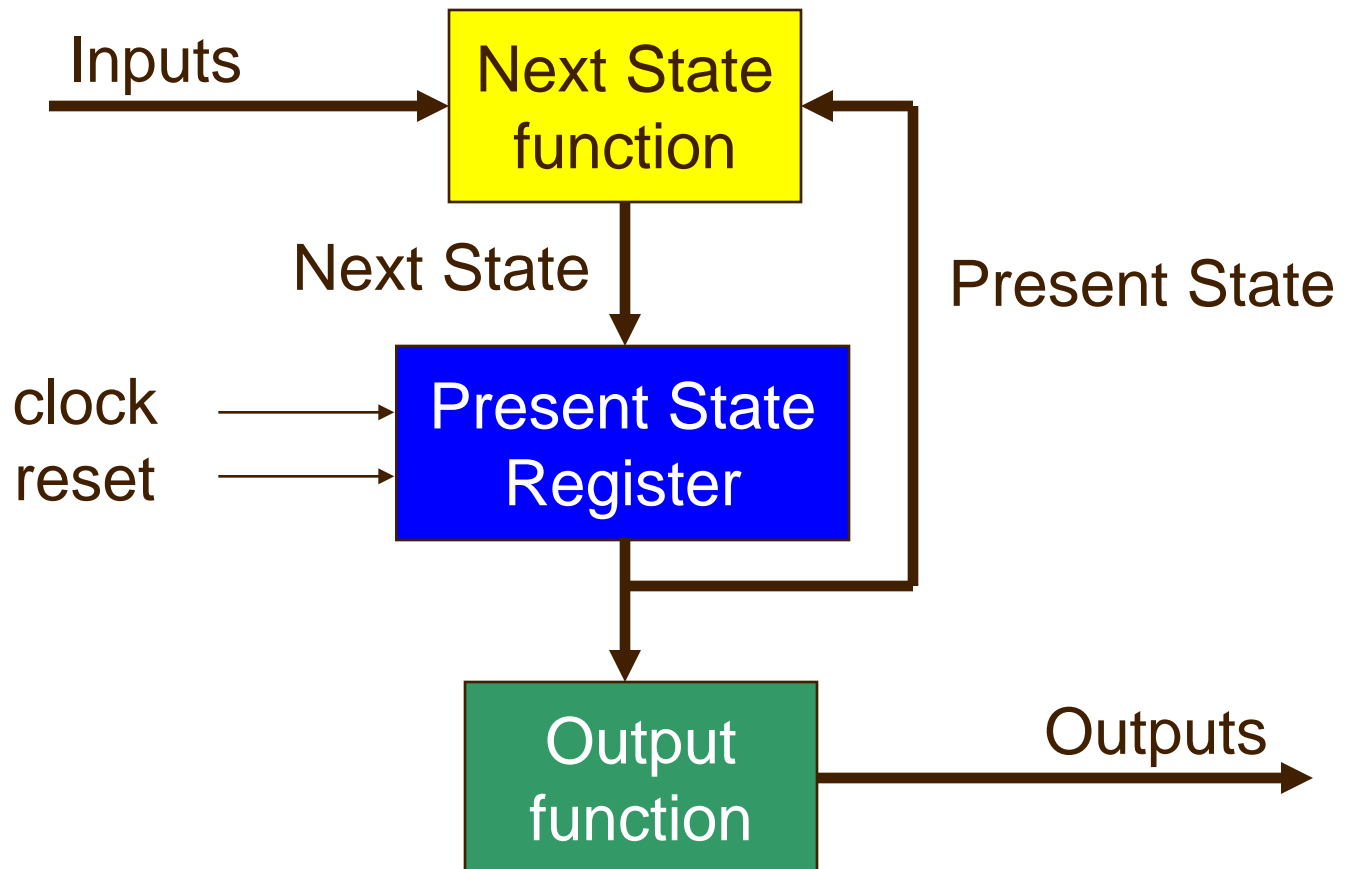- Η έξοδος είναι συνάρτηση μόνο της παρούσας κατάστασης




Mealy FSM

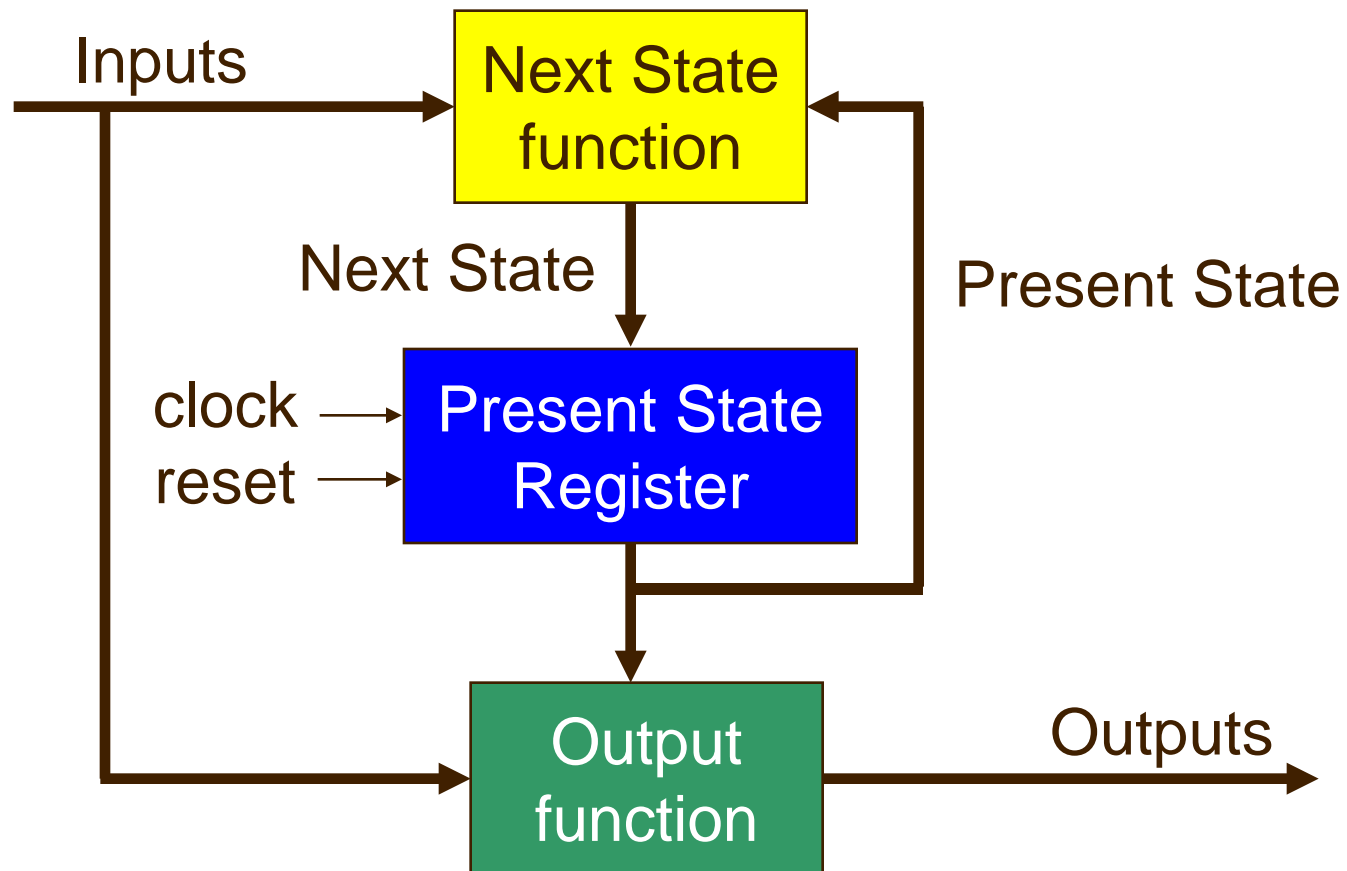
- Η έξοδος είναι συνάρτηση της παρούσας κατάστασης και των εισόδων



Moore Machine

 

Mealy Machine

 

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs μπορεί να είναι λειτουργικά ισοδύναμες
 - Μία ισοδύναμη Mealy FSM μπορεί να παραχθεί από μία Moore FSM και αντίστροφα
- Η τύπου Mealy FSM συνήθως απαιτεί λιγότερο αριθμό καταστάσεων
 - Το κύκλωμα απαιτεί λιγότερο χώρο

Moore vs. Mealy FSM (2)

- Mealy FSM Computes Outputs as soon as Inputs Change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has No Combinational Path Between Inputs and Outputs
 - Moore FSM is more likely to have a shorter critical path

Moore FSM - Example 1

 - Σχεδιάστε μία Moore FSM να αναγνωρίζει την ακολουθία "10"




Ερμηνεία των states: **S0**: κανένα ψηφίο της ακολουθίας δεν αναγνωρίστηκε ακόμα

S1: "1"
Αναγνώριση του «1»

S2: "10"
Αναγνώριση !!

Mealy FSM - Example 1

 
- Mealy FSM that Recognizes Sequence “10”



Meaning of states:

S0: No elements of the sequence observed	S1: “1” observed
--	------------------

Moore & Mealy FSMs – Example 1

 


FSMs σε VHDL

- Οι μηχανές πεπερασμένων καταστάσεων περιγράφονται με την βοήθεια *processes*.
- Τα εργαλεία Synthesis καταλαβαίνουν μία περιγραφή FSM αν ακολουθούνται κάποιοι κανόνες:
 - Οι μεταβάσεις καταστάσεων πρέπει να περιγράφονται μέσα σε ένα *process* sensitive στο *clock* and *asynchronous reset* signals **only**
 - Οι έξοδοι περιγράφονται ως παράλληλες εντολές (*statements*) έξω από ένα *process*


Moore FSM

process(clock, reset)

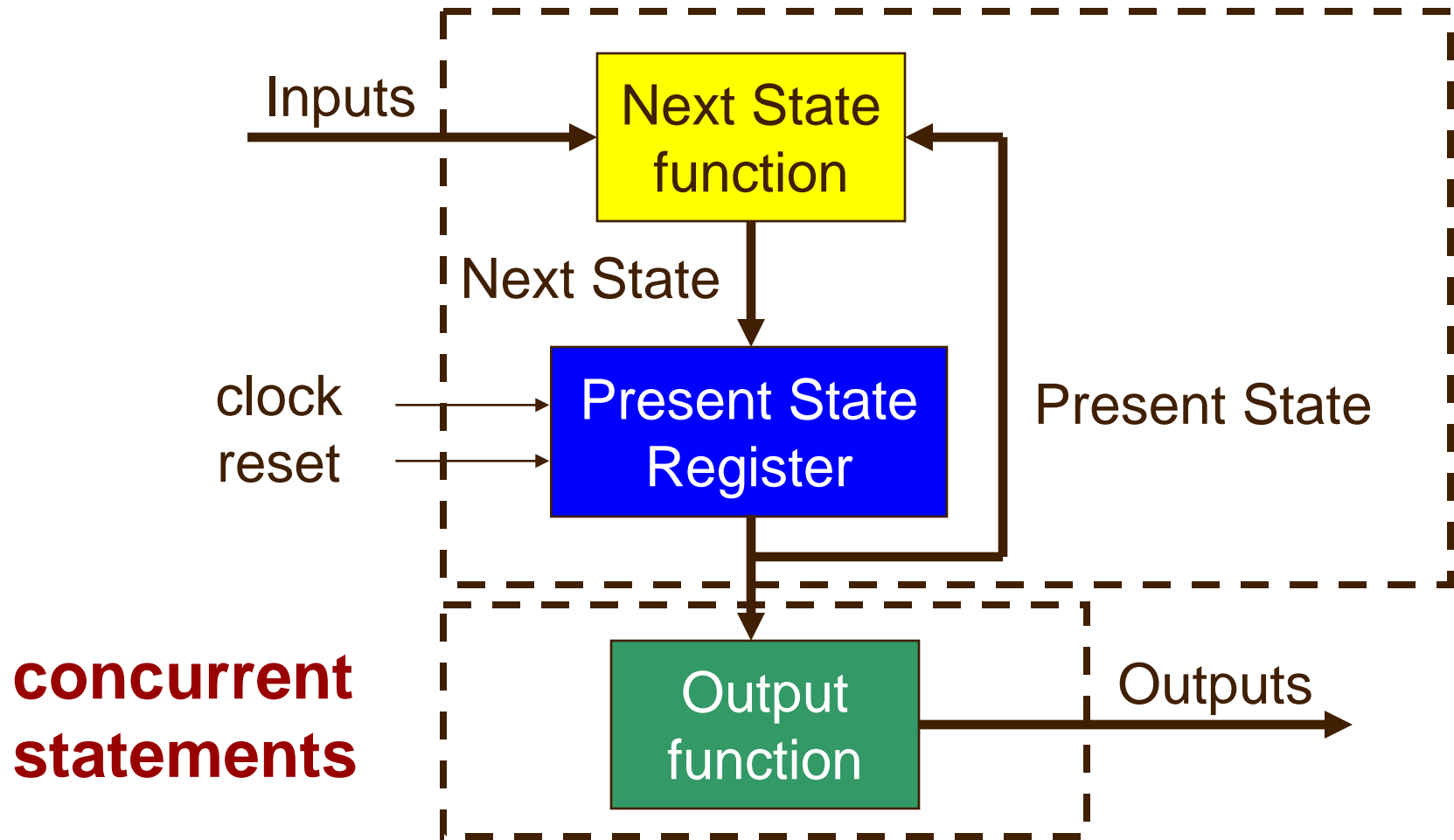

Mealy FSM


process(clock, reset)

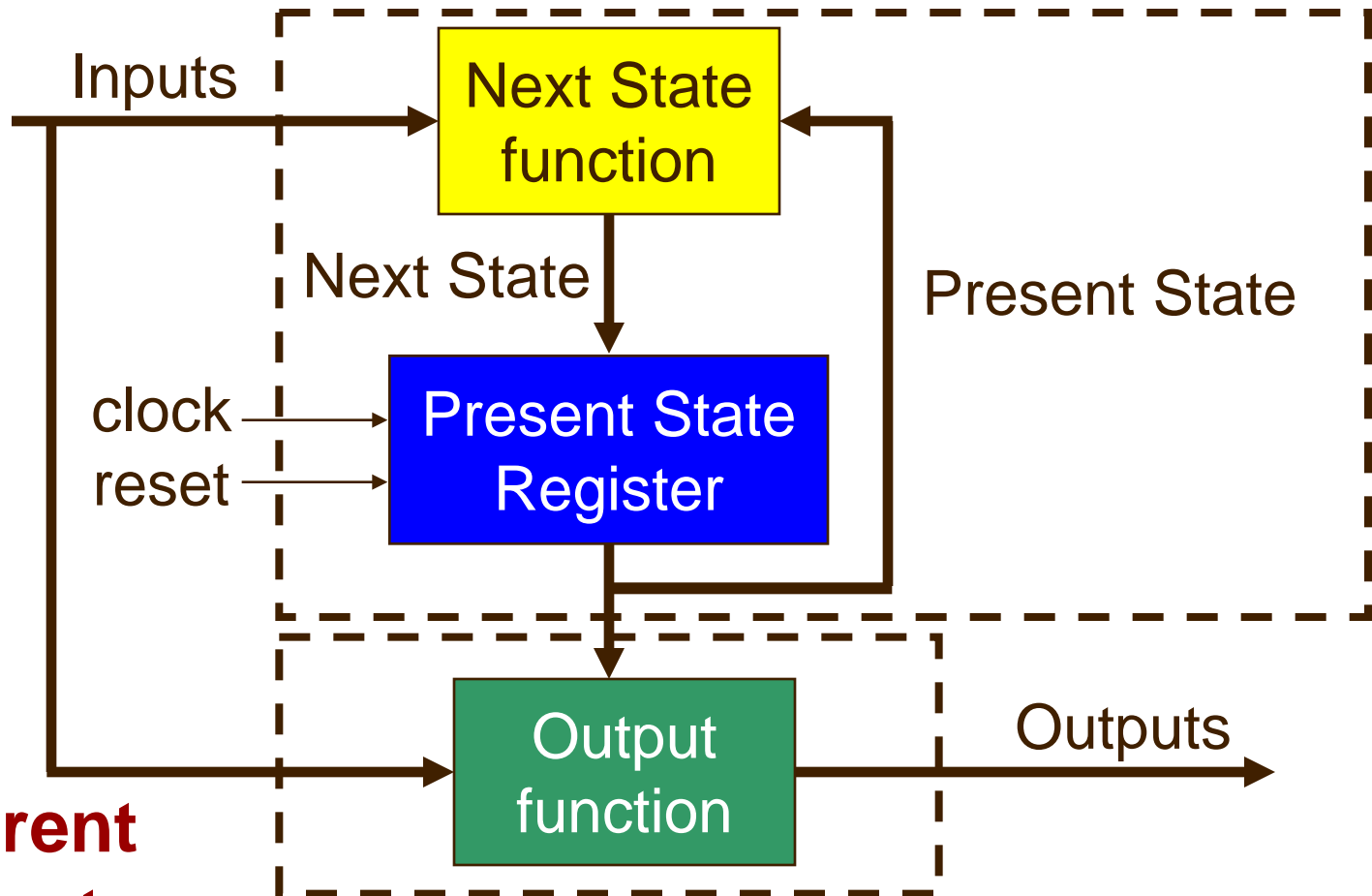

**concurrent
statements**

Moore FSM - Example 1

 - Moore FSM that Recognizes Sequence “10”



Moore FSM in VHDL (1)

```
TYPE state IS (S0, S1, S2);  
SIGNAL Moore_state: state;
```

```
U_Moore: PROCESS (clock, reset)  
BEGIN  
    IF(reset = '1') THEN  
        Moore_state <= S0;  
    ELSIF (clock = '1' AND clock'event) THEN  
        CASE Moore_state IS  
            WHEN S0 =>  
                IF input = '1' THEN  
                    Moore_state <= S1;  
                ELSE  
                    Moore_state <= S0;  
                END IF;  
        END CASE;  
    END IF;
```


Moore FSM in VHDL (2)

```
    WHEN S1 =>
        IF input = '0' THEN
            Moore_state <= S2;
        ELSE
            Moore_state <= S1;
        END IF;
    WHEN S2 =>
        IF input = '0' THEN
            Moore_state <= S0;
        ELSE
            Moore_state <= S1;
        END IF;
END CASE;
END IF;
END PROCESS;

Output <= '1' WHEN Moore_state = S2 ELSE '0';
```

Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”



Mealy FSM in VHDL (1)

```
TYPE state IS (S0, S1);  
SIGNAL Mealy_state: state;
```


```
U_Mealy: PROCESS(clock, reset)  
BEGIN  
    IF(reset = '1') THEN  
        Mealy_state <= S0;  
    ELSIF (clock = '1' AND clock'event) THEN  
        CASE Mealy_state IS  
            WHEN S0 =>  
                IF input = '1' THEN  
                    Mealy_state <= S1;  
                ELSE  
                    Mealy_state <= S0;  
                END IF;  
        END CASE;  
    END IF;
```

Mealy FSM in VHDL (2)

```
        WHEN S1 =>
            IF input = '0' THEN
                Mealy_state <= S0;
            ELSE
                Mealy_state <= S1;
            END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN (Mealy_state = S1 AND input = '0') ELSE '0';
```

Moore FSM – Example 2: State diagram

 


Moore FSM – Example 2: State table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Moore FSM

process(clock, reset)

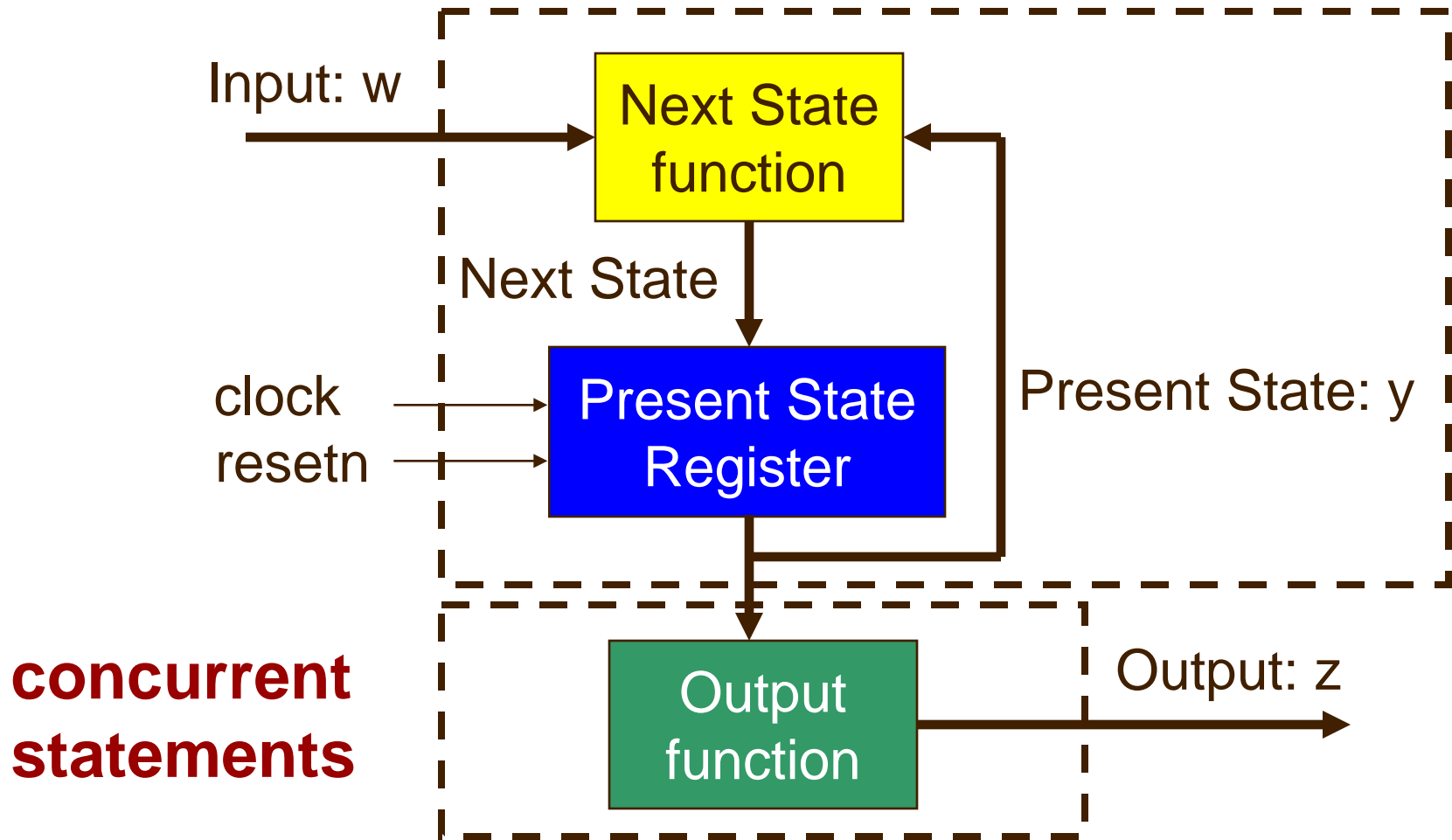

Moore FSM – Example 2: VHDL code (1)

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT ( clock  : IN STD_LOGIC ;  
          resetn  : IN STD_LOGIC ;  
          w       : IN STD_LOGIC ;  
          z       : OUT STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;  
    SIGNAL y : State_type ;
```

```
BEGIN
```

```
    PROCESS ( resetn, clock )
```

```
    BEGIN
```

```
        IF resetn = '0' THEN
```

```
            y <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

Moore FSM – Example 2: VHDL code (2)

```
CASE y IS
    WHEN A =>
        IF w = '0' THEN
            y <= A ;
        ELSE
            y <= B ;
        END IF ;
    WHEN B =>
        IF w = '0' THEN
            y <= A ;
        ELSE
            y <= C ;
        END IF ;
    WHEN C =>
        IF w = '0' THEN
            y <= A ;
        ELSE
            y <= C ;
        END IF ;
END CASE ;

END IF ;
END PROCESS ;

z <= '1' WHEN y = C ELSE '0' ;


END Behavior ;
```

Moore FSM

process
(w,
y_present)

process
(clock,
resetn)

concurrent
statements

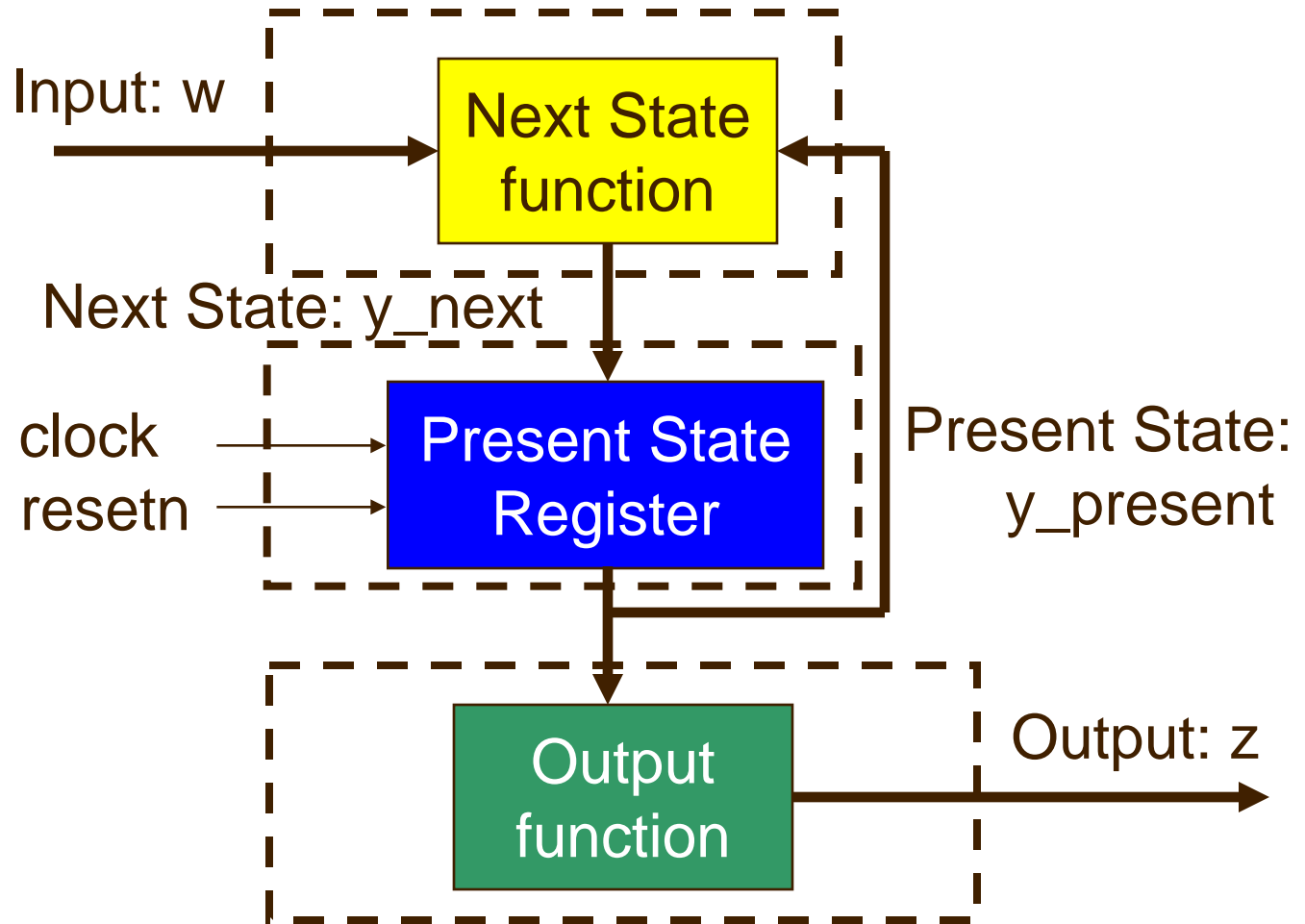

Alternative VHDL code (1)

```
ARCHITECTURE Behavior OF simple IS
  TYPE State_type IS (A, B, C) ;
  SIGNAL y_present, y_next : State_type ;
BEGIN
  PROCESS ( w, y_present )
  BEGIN
    CASE y_present IS
      WHEN A =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= B ;
        END IF ;
      WHEN B =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= C ;
        END IF ;
```


Alternative VHDL code (2)

```
        WHEN C =>
            IF w = '0' THEN
                y_next <= A ;
            ELSE
                y_next <= C ;
            END IF ;
        END CASE ;
    END PROCESS ;

PROCESS (clock, resetn)
BEGIN
    IF resetn = '0' THEN
        y_present <= A ;
    ELSIF (clock'EVENT AND clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

Mealy FSM – Example 2: State diagram

 


Mealy FSM – Example 2: State table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Mealy FSM

process(clock, reset)

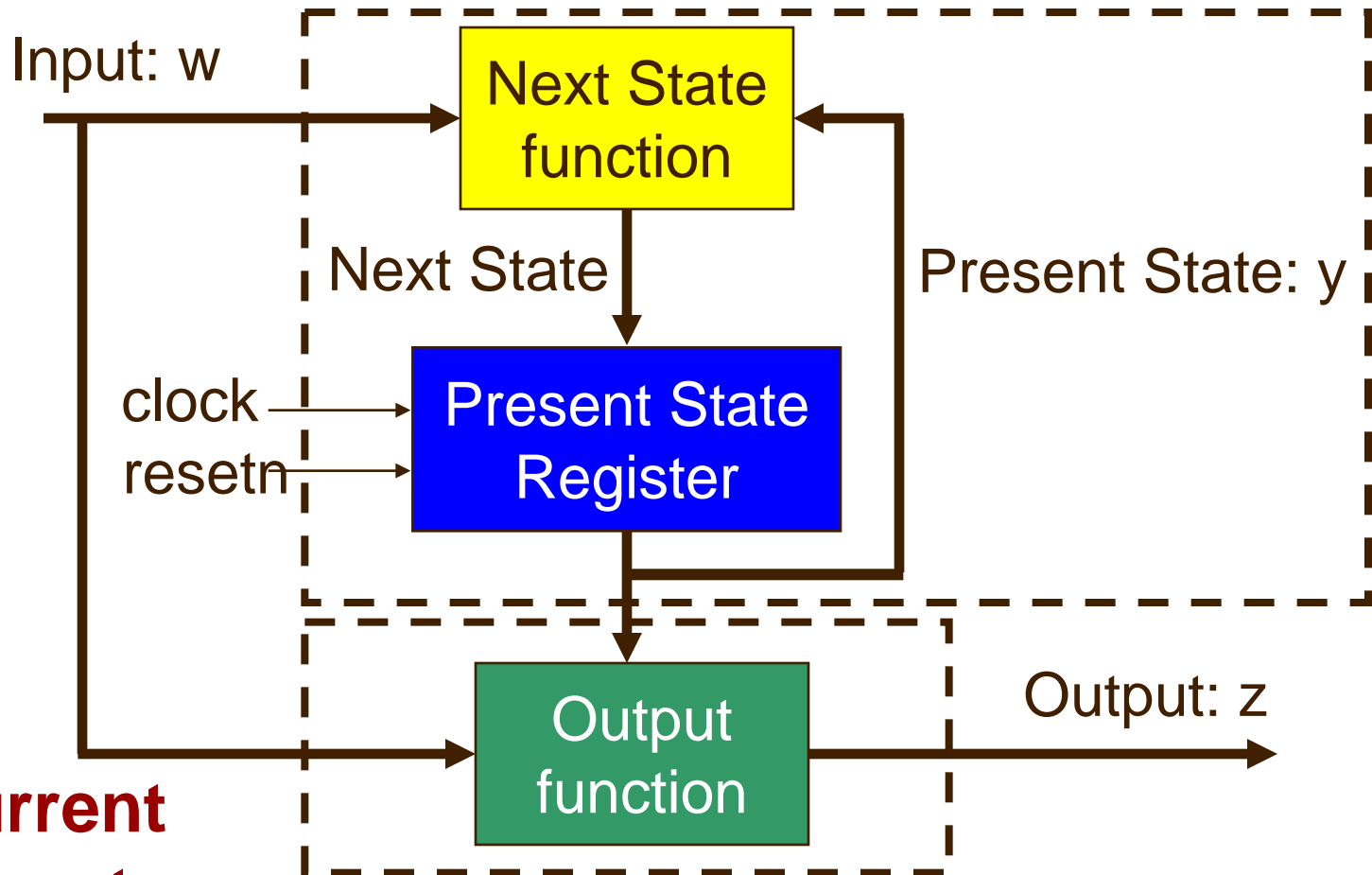

**concurrent
statements**

Mealy FSM – Example 2: VHDL code (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY Mealy IS
    PORT ( clock      : IN      STD_LOGIC ;
          resetn     : IN      STD_LOGIC ;
          w           : IN      STD_LOGIC ;
          z           : OUT     STD_LOGIC ) ;
END Mealy ;

ARCHITECTURE Behavior OF Mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( resetn, clock )
    BEGIN
        IF resetn = '0' THEN
            y <= A ;
        ELSIF (clock'EVENT AND clock = '1') THEN
```

Mealy FSM – Example 2: VHDL code (2)

```
CASE y IS
  WHEN A =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
  WHEN B =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
END CASE ;
```

Mealy FSM – Example 2: VHDL code (3)

```
    END IF ;  
END PROCESS ;
```

```
WITH y SELECT  
    z <= w WHEN B,  
    z <= '0' WHEN others;
```

```
END Behavior ;
```

State Encoding

State Encoding Problem

- State Encoding Can Have a Big Influence on Optimality of the FSM Implementation
 - No methods other than checking all possible encodings are known to produce optimal circuit
 - Feasible for small circuits only
- Using Enumerated Types for States in VHDL Leaves Encoding Problem for Synthesis Tool

Types of State Encodings (1)

- Binary (Sequential) – States Encoded as Consecutive Binary Numbers
 - Small number of used flip-flops
 - Potentially complex transition functions leading to slow implementations
- One-Hot – Only One Bit Is Active
 - Number of used flip-flops as big as number of states
 - Simple and fast transition functions
 - Preferable coding technique in FPGAs

Types of State Encodings (2)

State	Binary Code	One-Hot Code
S0	000	10000000
S1	001	01000000
S2	010	00100000
S3	011	00010000
S4	100	00001000
S5	101	00000100
S6	110	00000010
S7	111	00000001

A user-defined attribute for manual state assignment

(ENTITY declaration not shown)

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;
```

```
    ATTRIBUTE ENUM_ENCODING
```

```
    : STRING ;
```

```
    ATTRIBUTE ENUM_ENCODING OF State_type
```

```
    : TYPE IS "00 01 11" ;
```

```
    SIGNAL y_present, y_next : State_type ;
```

```
BEGIN
```

con't ...

Using constants for manual state assignment (1)

```
ARCHITECTURE Behavior OF simple IS
```

```
    SUBTYPE ABC_STATE is STD_LOGIC_VECTOR(1 DOWNT0 0);
```

```
    CONSTANT A : ABC_STATE := "00" ;
```

```
    CONSTANT B : ABC_STATE := "01" ;
```

```
    CONSTANT C : ABC_STATE := "11" ;
```

```
    SIGNAL y_present, y_next : ABC_STATE;
```

```
BEGIN
```

```
    PROCESS ( w, y_present )
```

```
    BEGIN
```

```
        CASE y_present IS
```

```
            WHEN A =>
```

```
                IF w = '0' THEN y_next <= A ;
```

```
                ELSE y_next <= B ;
```



```
                END IF ;
```

```
... con't
```

Clock Process Example

```

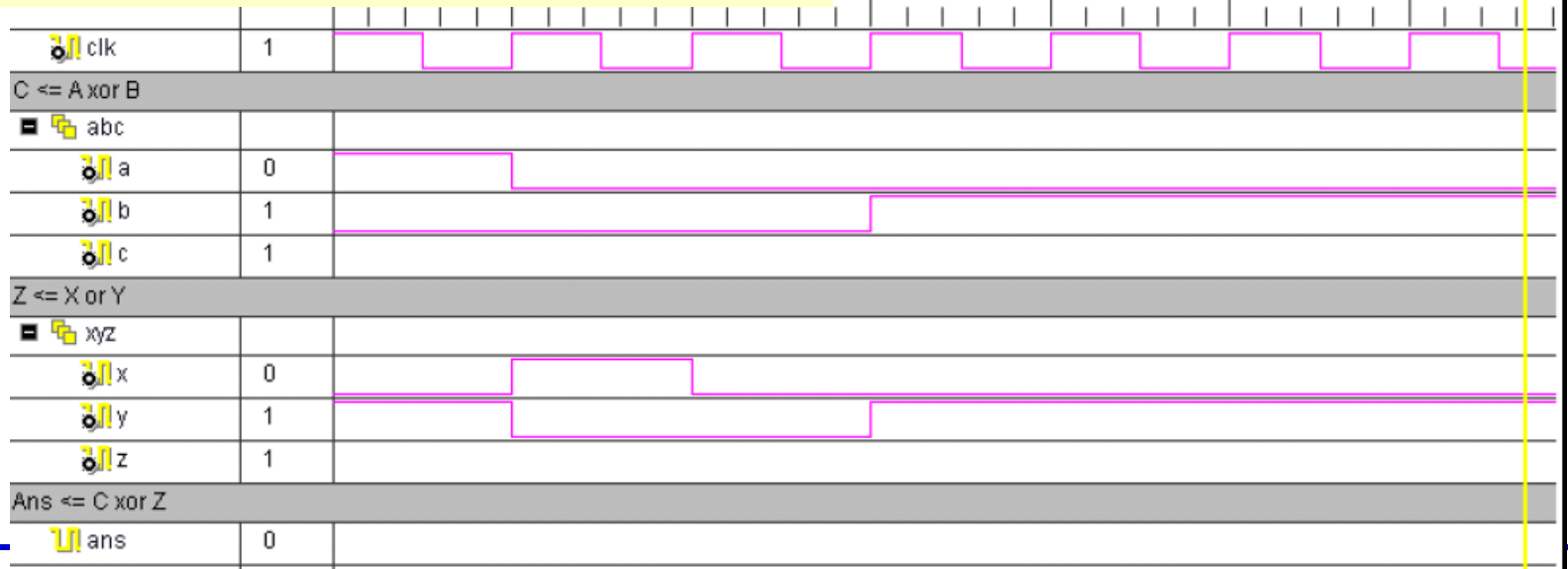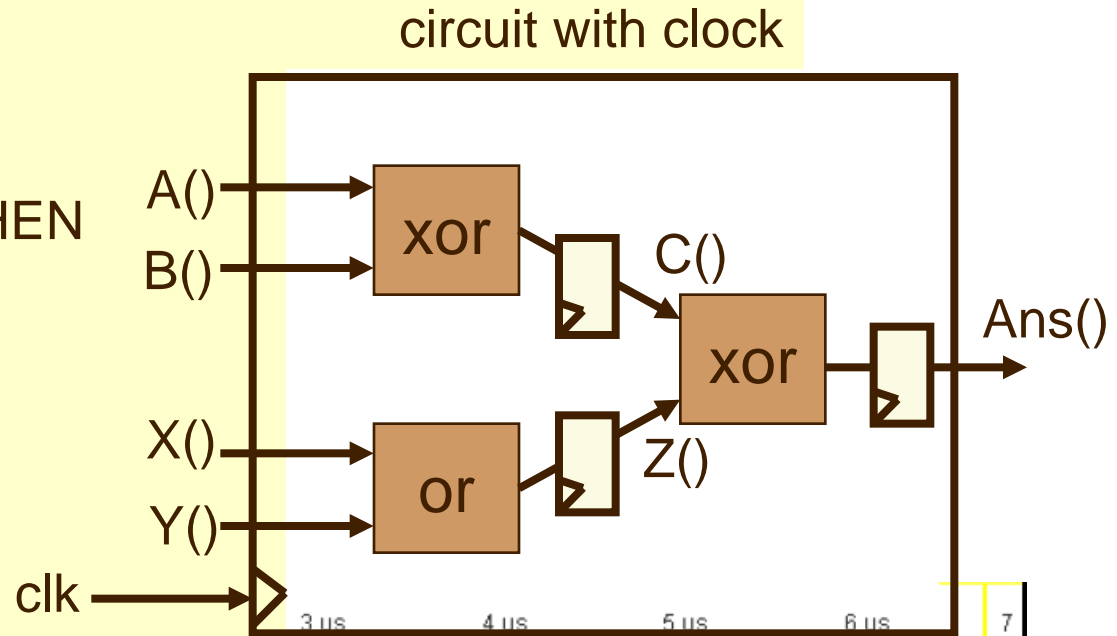BEGIN
  My_process_1 : process (clk)
  Begin
    IF (clk'event and clk = '1') THEN
      C <= A xor B;
      Z <= X or Y;
      Ans <= C xor Z;
    END IF;
  End My_process_1;
END;
  
```



Clock Process Example (Answer)

BEGIN

My_process_1 : process (clk)

Begin

IF (clk'event and clk = '1') THEN

C <= A xor B;

Z <= X or Y;

Ans <= C xor Z;

END IF;

End My_process_1;

END;

circuit with clock

