

VHDL ακολουθιακή λογική

Λογική με στοιχεία μνήμης

DFF




clk	q*
0	q
1	q
⌋	d

(a) D FF



reset	clk	q*
1	-	0
0	0	q
0	1	q
0	⌋	d


(b) D FF with asynchronous reset

 

reset	clk	en	q*
1	-	-	0
0	0	-	q
0	1	-	q
0	⌋	0	q
0	⌋	1	d

Flip-Flop με Enable

Λογική ενός ασύγχρονου συστήματος

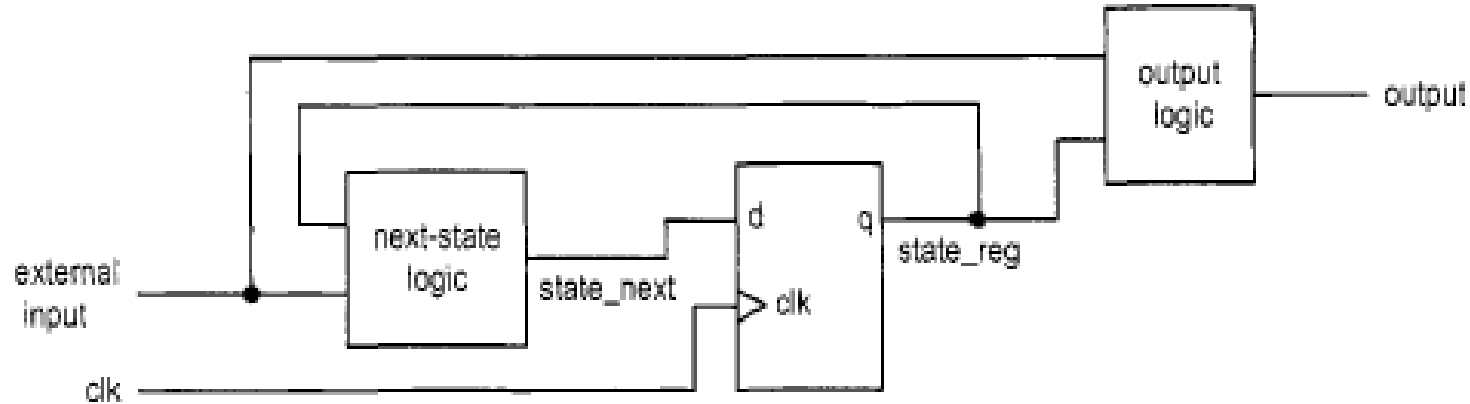


DFF με enable

```
library ieee;
use ieee.std_logic_1164.all;
entity d_ff_en is
    port(
5      clk, reset: in std_logic;
        en: in std_logic;
        d: in std_logic;
        q: out std_logic
    );
10 end d_ff_en;

    architecture arch of d_ff_en is
begin
    process (clk, reset)
15     begin
        if (reset='1') then
            q <='0';
        elsif (clk'event and clk='1') then
            if (en='1') then
20                q <= d;
            end if;
        end if;
    end process;
end arch;
```

DFF με enable (mux – dff)
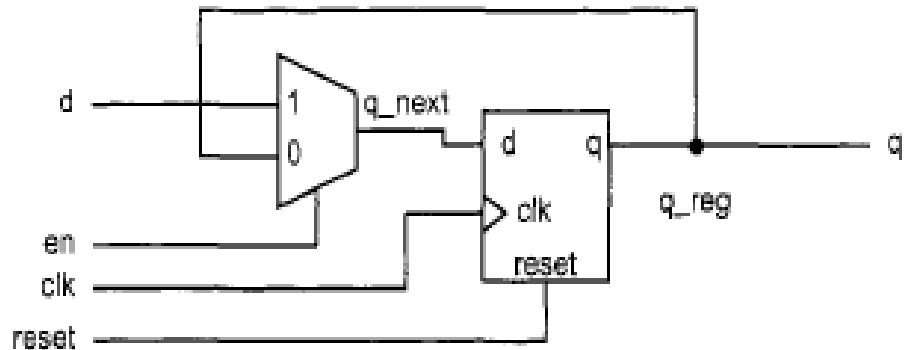
```
begin
  -- D FF
  process (clk, reset)
  begin
    if (reset='1') then
      r_reg <= '0';
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
  -- next-state logic
  r_next <= d when en = '1' else
  10   r_reg;
  -- output logic
  q <= r_reg;
end two_seg_arch;
```



Register

```
library ieee;
use ieee.std_logic_1164.all;
entity reg_reset is
    port(
6       clk, reset: in std_logic;
        d: in std_logic_vector(7 downto 0);
        q: out std_logic_vector(7 downto 0)
    );
end reg_reset;


architecture arch of reg_reset is
begin
    process(clk, reset)
    begin
15        if (reset='1') then
            q <=(others=>'0');
            elsif (clk'event and clk='1') then
                q <= d;
            end if;
20    end process;
end arch;
```

Shift Register

```
library ieee;
use ieee.std_logic_1164.all;
entity free_run_shift_reg is
  generic(N: integer := 8);
5  port(
    clk, reset: in std_logic;
    s_in: in std_logic;
    s_out: out std_logic
  );
10 end free_run_shift_reg;

architecture arch of free_run_shift_reg is
  signal r_reg: std_logic_vector(N-1 downto 0);
  signal r_next: std_logic_vector(N-1 downto 0);
15 begin
  -- register
  process(clk,reset)
  begin
    if (reset='1') then
20     r_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      r_reg <= r_next;
    end if;
  end process;
25 -- next-state logic (shift right 1 bit)
  r_next <= s_in & r_reg(N-1 downto 1);
  -- output
  s_out <= r_reg(0);
end arch;
```

Μετρητής BCD


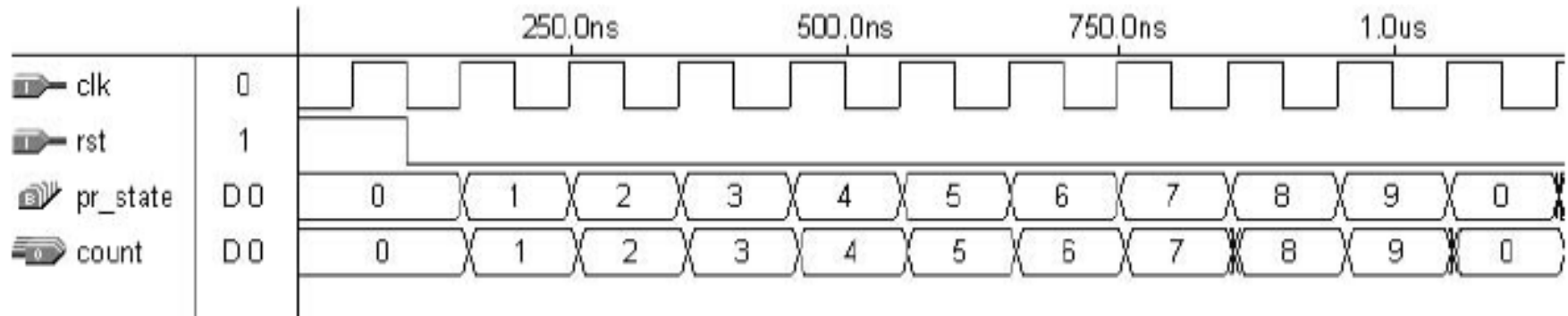


```
1 -----  
2 LIBRARY ieee;  
3 USE ieee.std_logic_1164.all;  
4 -----  
5 ENTITY counter IS  
6     PORT ( clk, rst: IN STD_LOGIC;  
7           count: OUT STD_LOGIC_VECTOR (3 DOWNTO 0));  
8 END counter;  
9 -----
```

Μετρητής BCD (architecture)

```
10 ARCHITECTURE state_machine OF counter IS
11     TYPE state IS (zero, one, two, three, four,
12         five, six, seven, eight, nine);
13     SIGNAL pr_state, nx_state: state;
14 BEGIN
15     ----- Lower section: -----
16     PROCESS (rst, clk)
17     BEGIN
18         IF (rst='1') THEN
19             pr_state <= zero;
20         ELSIF (clk'EVENT AND clk='1') THEN
21             pr_state <= nx_state;
22         END IF;
23     END PROCESS;
24     ----- Upper section: -----
25     PROCESS (pr_state)
26     BEGIN
27         CASE pr_state IS
28             WHEN zero =>
29                 count <= "0000";
30                 nx_state <= one;
31             WHEN one =>
32                 count <= "0001";
33                 nx_state <= two;
34                 WHEN two =>
35                     count <= "0010";
36                     nx_state <= three;
37                 WHEN three =>
38                     count <= "0011";
39                     nx_state <= four;
40                 WHEN four =>
41                     count <= "0100";
42                     nx_state <= five;
43                 WHEN five =>
44                     count <= "0101";
45                     nx_state <= six;
46                 WHEN six =>
47                     count <= "0110";
48                     nx_state <= seven;
49                 WHEN seven =>
50                     count <= "0111";
51                     nx_state <= eight;
52                 WHEN eight =>
53                     count <= "1000";
54                     nx_state <= nine;
55                 WHEN nine =>
56                     count <= "1001";
57                     nx_state <= zero;
58             END CASE;
59     END PROCESS;
60 END state_machine;
61 -----
```

Απλή FSM

 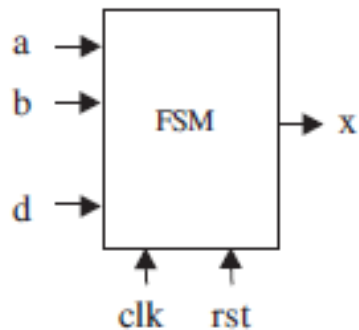



```
1 -----  
2 ENTITY simple_fsm IS  
3     PORT ( a, b, d, clk, rst: IN BIT;  
4           x: OUT BIT);  
5 END simple_fsm;  
6 -----
```

Απλή FSM (architecture)



```

7 ARCHITECTURE simple_fsm OF simple_fsm IS
8   TYPE state IS (stateA, stateB);
9   SIGNAL pr_state, nx_state: state;
10 BEGIN
11   ----- Lower section: -----
12   PROCESS (rst, clk)
13   BEGIN
14     IF (rst='1') THEN
15       pr_state <= stateA;
16     ELSIF (clk'EVENT AND clk='1') THEN
17       pr_state <= nx_state;
18     END IF;
19   END PROCESS;
20   ----- Upper section: -----
21   PROCESS (a, b, d, pr_state)
22   BEGIN
23     CASE pr_state IS
24       WHEN stateA =>
25         x <= a;
26         IF (d='1') THEN nx_state <= stateB;
27         ELSE nx_state <= stateA;
28         END IF;
29       WHEN stateB =>
30         x <= b;
31         IF (d='1') THEN nx_state <= stateA;
32         ELSE nx_state <= stateB;
33         END IF;
34     END CASE;
35   END PROCESS;
36 END simple_fsm;

```

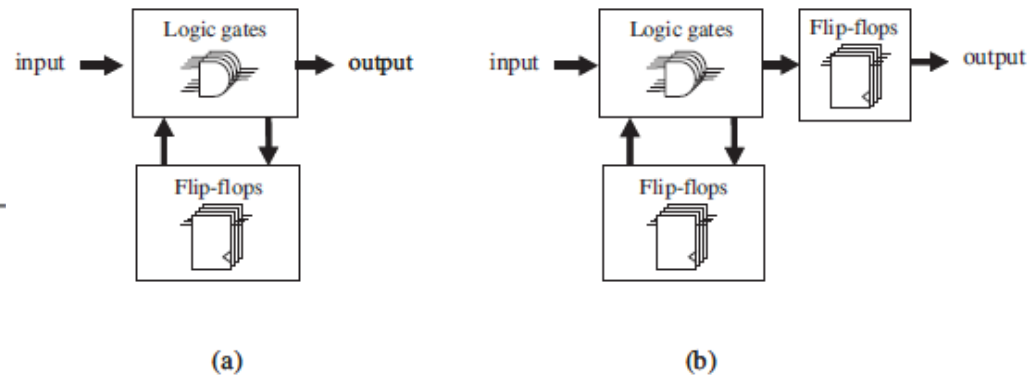 

FSM Παραδείγματα

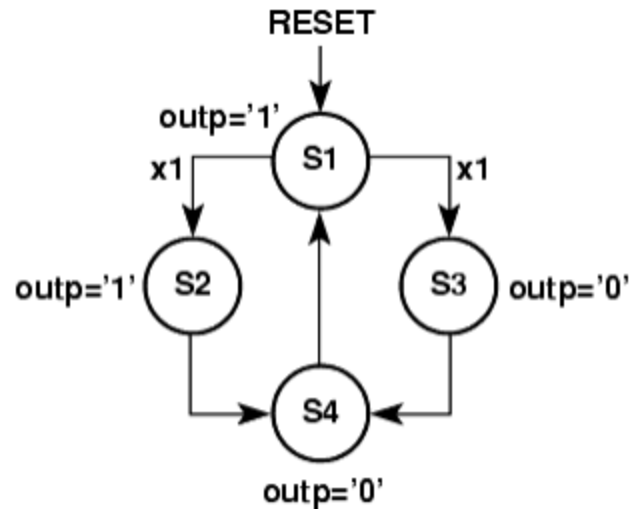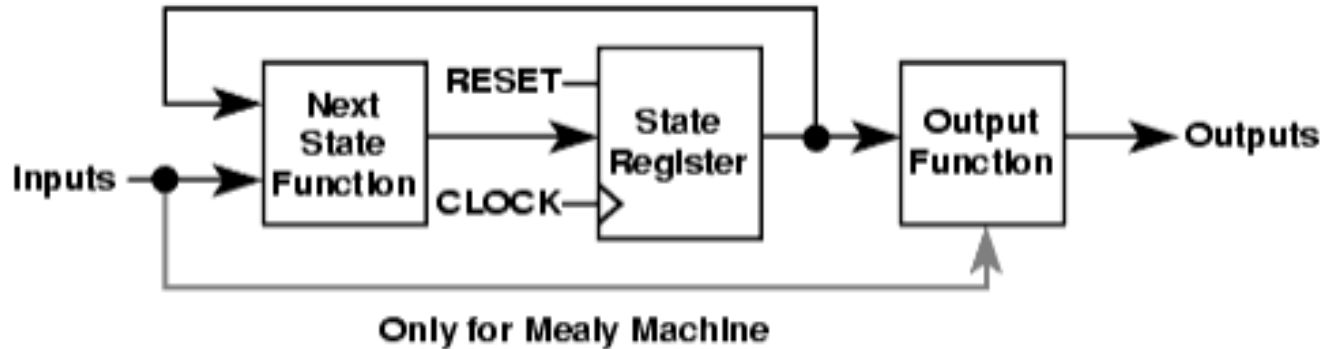


```

library IEEE;
use IEEE.std_logic_1164.all;

entity fsm is
  port ( clk, reset, x1 : IN std_logic;
         outp : OUT std_logic);
end entity;
architecture beh1 of fsm is
  type state_type is (s1,s2,s3,s4);
  signal state: state_type ;
begin
  process (clk,reset)
  begin
    if (reset ='1') then
      state <=s1; outp<='1';
    elsif (clk='1' and clk'event) then
      case state is
        when s1 => if x1='1' then state <= s2;
                   else      state <= s3;
                   end if;
        when s2 => state <= s4; outp <= '1';
        when s3 => state <= s4; outp <= '0';
        when s4 => state <= s1; outp <= '0';
      end case;
    end if;
  end process;
end beh1;

```

FSM with 2 processes

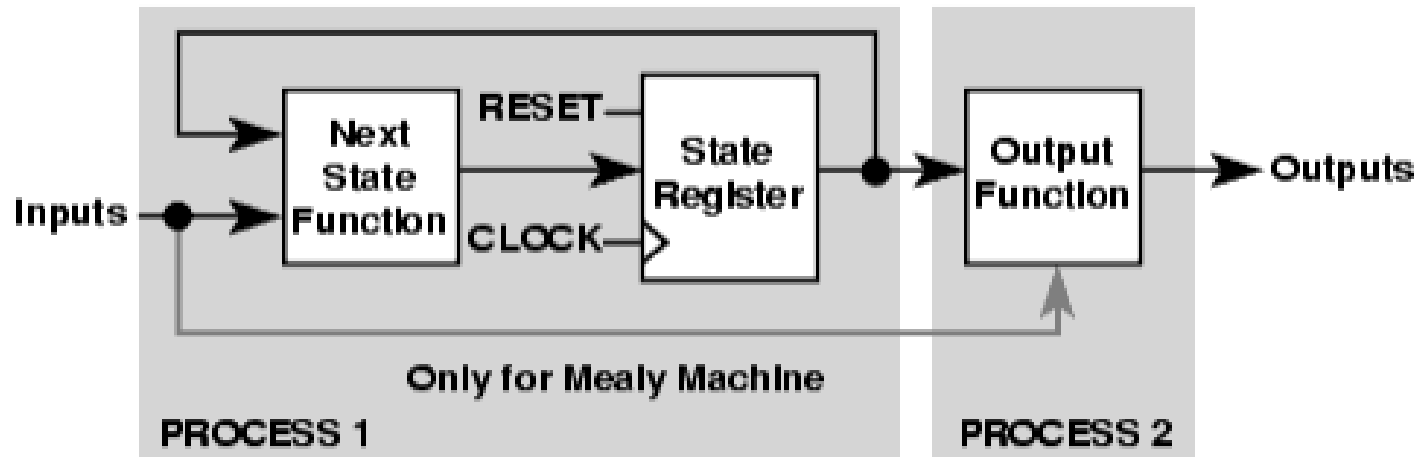


```
library IEEE;
use IEEE.std_logic_1164.all;

entity fsm is
    port ( clk, reset, x1 : IN std_logic;
          outp : OUT std_logic);
end entity;
architecture beh1 of fsm is
    type state_type is (s1,s2,s3,s4);
    signal state: state_type ;
begin
    process1: process (clk,reset)
    begin
        if (reset ='1') then state <=s1;
        elsif (clk='1' and clk'Event) then
            case state is
                when s1 => if x1='1' then state <= s2;
                           else state <= s3;
                           end if;
                when s2 => state <= s4;
                when s3 => state <= s4;
                when s4 => state <= s1;
            end case;
        end if;
    end process process1;
```

```
process2 : process (state)
begin
    case state is
        when s1 => outp <= '1';
        when s2 => outp <= '1';
        when s3 => outp <= '0';
        when s4 => outp <= '0';
    end case;
end process process2;
end beh1;
```

FSM with 3 processes

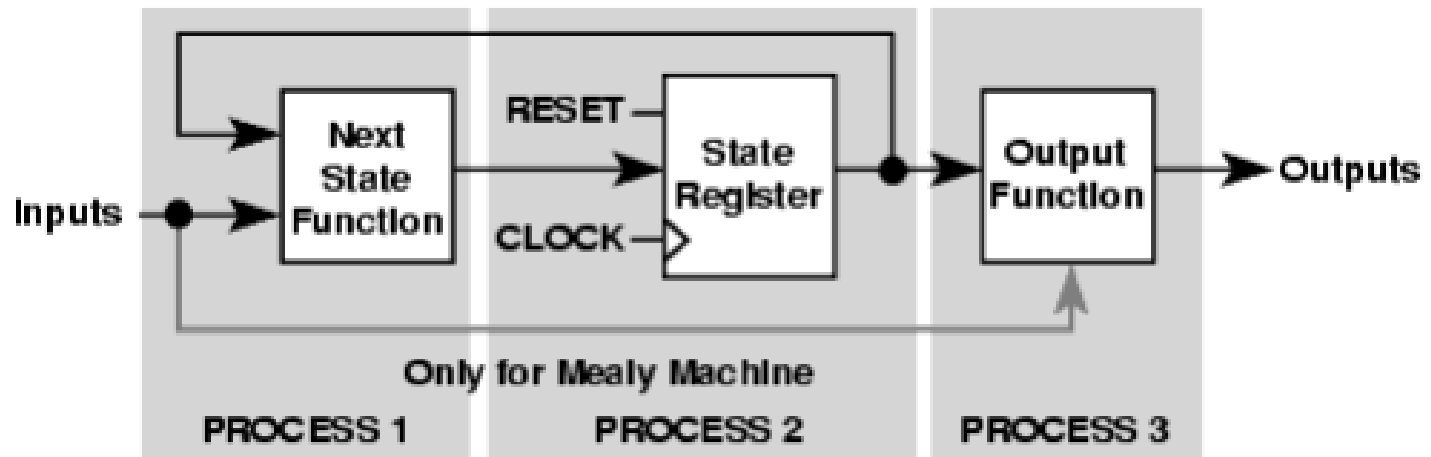

```

library IEEE;
use IEEE.std_logic_1164.all;

entity fsm is
  port ( clk, reset, x1 : IN std_logic;
         outp : OUT std_logic);
end entity;
architecture beh1 of fsm is
  type state_type is (s1,s2,s3,s4);
  signal state, next_state: state_type ;
begin
  process1: process (clk,reset)
  begin
    if (reset ='1') then
      state <=s1;
    elsif (clk='1' and clk'Event) then
      state <= next_state;
    end if;
  end process process1;

```

```

  process2 : process (state, x1)
  begin
    case state is
      when s1 => if x1='1' then
                    next_state <= s2;
                  else
                    next_state <= s3;
                  end if;
      when s2 => next_state <= s4;
      when s3 => next_state <= s4;
      when s4 => next_state <= s1;
    end case;
  end process process2;

  process3 : process (state)
  begin
    case state is
      when s1 => outp <= '1';
      when s2 => outp <= '1';
      when s3 => outp <= '0';
      when s4 => outp <= '0';
    end case;
  end process process3;
end beh1;

```

```

library ieee;
    use ieee.std_logic_1164.all;
entity lfsr is
port (
    cout  :out std_logic_vector (7 downto 0);-- Output of the counter
    enable :in  std_logic;           -- Enable counting
    clk   :in  std_logic;           -- Input rlock
    reset :in  std_logic   );
end entity;
architecture rtl of lfsr is
    signal count      :std_logic_vector (7 downto 0);
    signal linear_feedback :std_logic;
begin
    linear_feedback <= not(count(7) xor count(3));

    process (clk, reset) begin
        if (reset = '1') then
            count <= (others=>'0');
        elsif (rising_edge(clk)) then
            if (enable = '1') then
                count <= (count(6) & count(5) & count(4) & count(3) & count(2) & count(1) & count(0) & linear_feedback);
            end if;
        end if;
    end process;
    cout <= count;
end architecture;

```