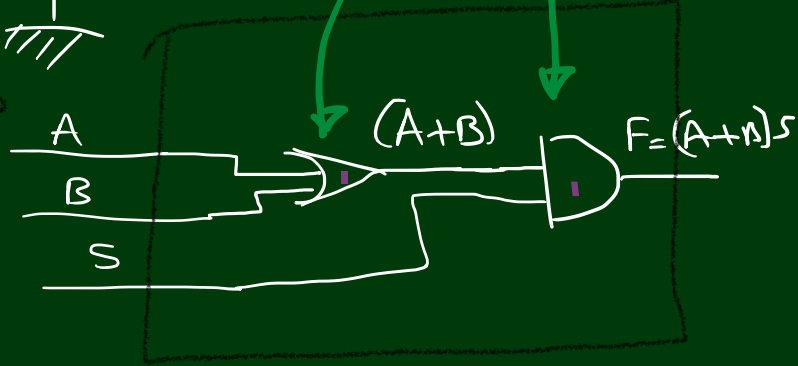


ΑΓΙΟΥ ΒΥ
ΣΥΝΑΓΕΡΤΩΣ


$$F = (A+B) \cdot S$$

$$= S(A+B)$$



$$F = (A+B) \cdot S$$


NAND

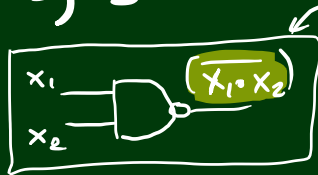


$$(\overline{\overline{A}} = A) \quad A \text{ --- } \text{NOT} \text{ --- } \overline{A}$$

(De Morgan)

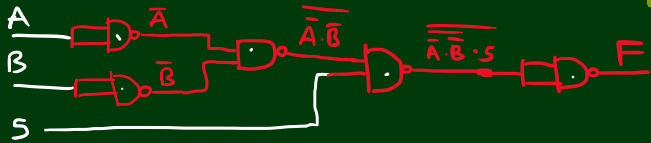
$$F = (A+B) \cdot S = \overline{\overline{(A+B)}} \cdot S = \overline{\overline{A} \cdot \overline{B}} \cdot S = \overline{\overline{A} \cdot \overline{B}} \cdot S$$






NOR

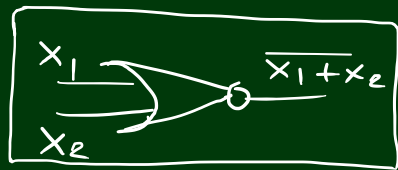
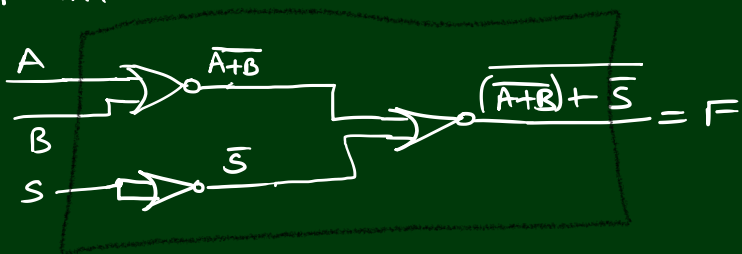
$$F = (A+B) \cdot S = \overline{\overline{(A+B) \cdot S}} = \overline{\overline{(A+B)} + \overline{S}}$$






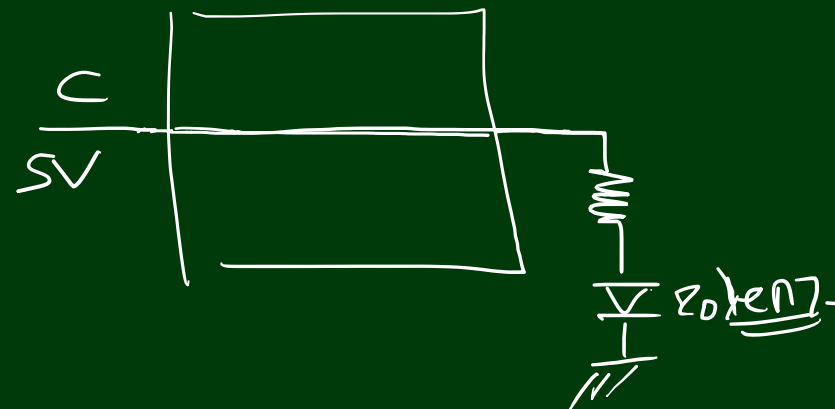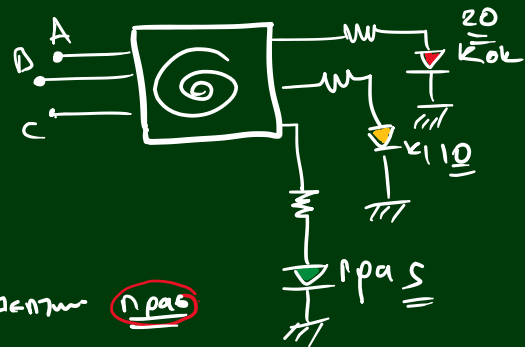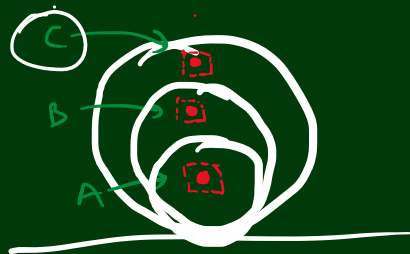


$A \cdot \bar{B} \cdot \bar{C} = F_1$ 52kΩм 1pas
 $L \cdot \bar{0} \cdot \bar{0} = L \cdot 1 \cdot 1 = L$

$A \cdot B \cdot \bar{C} = F_2$ 101kΩм к17p

$A \cdot B \cdot C = F_3$ 201kΩм к0k

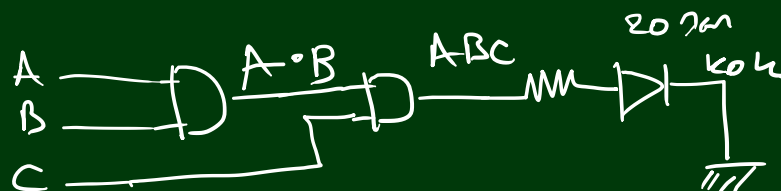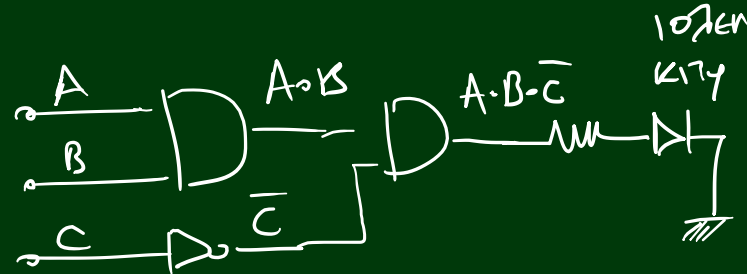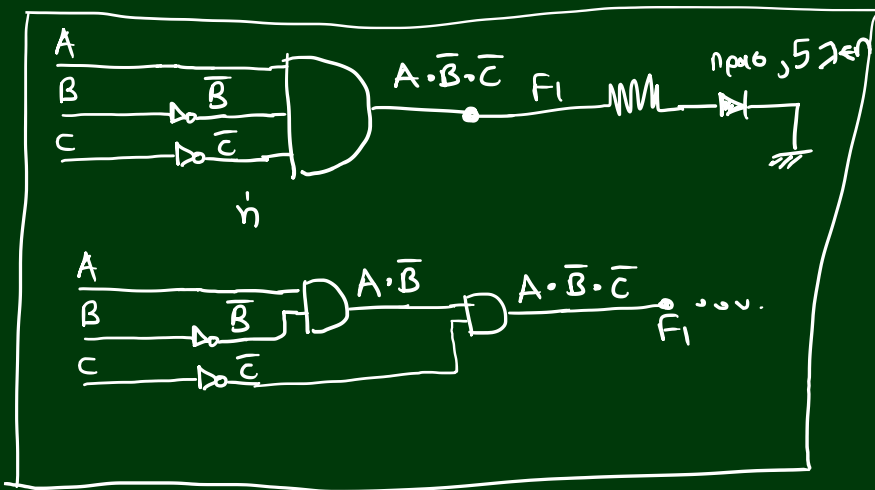

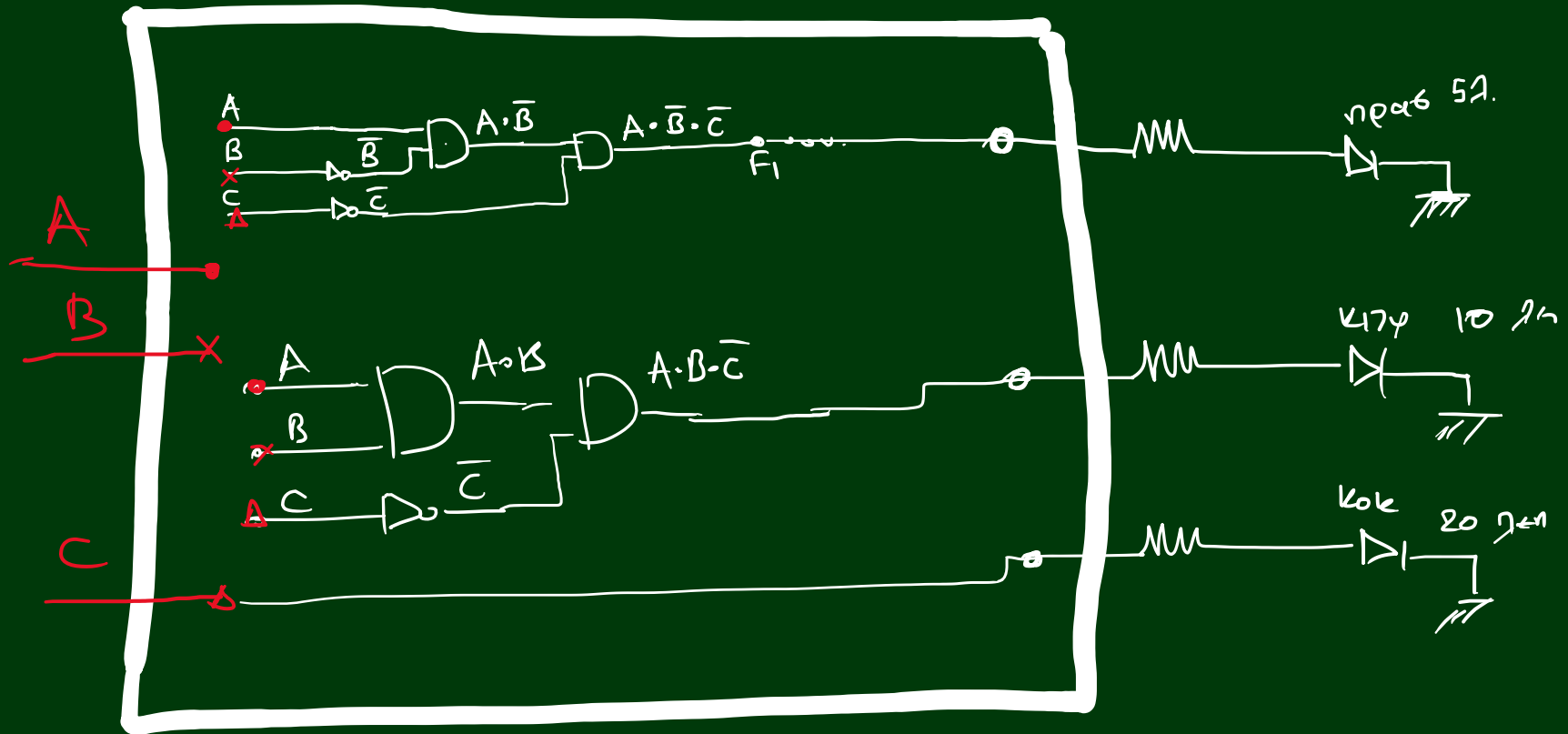

4 нУДЕА АНР → 1 0 0 0 0
 3 нУДЕА НОТ → 1 0 0 0 0

2 0 0 0 0

